

Total No. of printed pages = 5

END SEMESTER/RETEST EXAMINATION J/F

2023

Semester : 3rd

Branch : Common

Subject Code : El/Et - 304

FUNDAMENTALS OF ELECTRICAL AND ELECTRONICS ENGINEERING

Full Marks – 70

Time – Three hours

The figures in the margin indicate full marks
for the questions.

Instructions :

- All questions of PART – A are compulsory.
- Answer any five questions from PART – B.

PART – A

Marks – 25

1. Fill up the blanks : $1 \times 10 = 10$

(a) The property of substance for which it resists
the flow of electrons though it is called
_____.

(b) Conductivity is the reciprocal of _____.

[Turn over

(c) According to Ohm's law _____ is directly proportional to _____.

(d) At any junction the algebraic sum of current is _____.

(e) For an Ideal transformer VTR , $k = \dots$

(f) The emitter of a transistor is _____ doped.

(g) _____ is the rotating part of DC machine.

(h) The induced voltage in case of an electrical DC motor is called _____.

(i) NAND gate is the combination of NOT and _____ gate.

(j) _____ gate is also called as inverter.

2. Answer in *one* sentence/word each : $1 \times 10 = 10$

(i) How resistance of a conductor varies with cross-sectional area of the conductor ?

(ii) Give the unit of conductance.

(iii) Define transformer.

(iv) Define EMF.

(v) What is passive element ?

(vi) Define 1 A current.

(vii) What is the value of Indian frequency ?

(viii) How many terminals a transistor has ?

(ix) Define band gap energy.

(x) $Y = A \cdot B$, which gate is represented by this Boolean expression ?

3. Match the following :

$1 \times 5 = 5$

Column – A	Column – B
(a) One-half cycle	(i) Silicon
(b) Capacitance	(ii) OR gate
(c) Semiconductor	(iii) Henry
(d) $0+1=1$	(iv) Safety element
(e) Fuse	(v) Alternation

PART – B

Marks – 45

4. (a) What are the factors on which resistance of a conductor depends ? 3

(b) Three resistors are connected in series across a 12 V battery. The first resistor has a value of 1 Ohm, second has a voltage drop of 4V and third has a power dissipation of 12W. Calculate the value of current. 6

5. (a) What are the two types of self-excited DC generator? Draw the circuit diagram and explain. $1+2+2=5$

(b) An 8-pole DC shunt generator with 778 wave connected armature conductors and running at 500 rpm supplies a load of 12.5Ω resistance at terminal voltage of 250 volt. The armature resistance is 0.24Ω and field resistance is 250Ω . Find the armature current, induced emf and flux per pole. $1+1+2=4$

6. (a) Define the terms : $1 \times 3 = 3$

- (i) Time period,
- (ii) Frequency,
- (iii) Form factor.

(b) A resistance of 20Ω , an inductance of 0.2H and a capacitance of $100\mu\text{F}$ are connected in series across 220V , 50Hz mains. Calculate the current and voltage across R, L and C, impedance, power and power factor consumed by the circuit. 6

7. (a) Describe the P-N junction diode. 2

(b) Differentiate extrinsic semiconductor and intrinsic semiconductor. 3

(c) Explain the operation of PNP transistor. 4

8. (a) What is fuse ? Write the operation of fuse. $1+2=3$

(b) Mention four safety precaution rules required for electrical installation. 4

(c) Name four instruments used in electrical installation. 2

9. (a) What are the basics logic gates ? Draw the circuit diagram and truth table $2+3=5$

(b) What do you mean by Universal Logic gate. Write the Boolean expression and truth table of NAND gate. $1+1+2=4$

10. (a) Derive the EMF equation of DC generator. 3

(b) Establish the voltage equation of transformer. 4

(c) Write the current and voltage equation for alternating current. 2